

7. Explain the structure and working of n-Channel JFET and give its characteristics.
8. What is Pinch Off Voltage ? What is the structural difference between Enhancement and Depletion MOSFET ? $2 \times 5 = 10$

SECTION—C

9. Do any *five* :
- (i) Give the comparison between FET and BJT.
- (ii) What is a filter circuit ? Draw the circuit for pie filter.
- (iii) What is the relation between alpha and beta ?
- (iv) A d.c. voltage source having an open circuit voltage of 4V and internal resistance of 2 ohm. Obtain an equivalent current source.
- (v) Classify conductors, insulators and semiconductors on the basis of their Band Structure.
- (vi) What is the charge on a p-type semiconductor ? Explain.
- (vii) Can Emitter and Collector be interchanged. Explain.
- $5 \times 2 = 10$

Roll No.

Total No. of Pages : 2

PC 11485-NH

CS/2111

**ELECTRONIC—I : ELECTRONICS AND SOLID
STATE DEVICES, Paper—B
Semester—V**

Time Allowed : Three Hours]

[Maximum Marks : 30

Note :- The candidates are required to attempt *two* questions each from Sections A and B. Section C will be compulsory.

SECTION—A

1. Discuss Zener Diode and Zener Breakdown. Explain Voltage Stabilization by it.
2. Explain Half Wave Rectification. Derive expressions for Peak Inverse Voltage, Efficiency, V_{rms} .
3. What is a Voltage multiplier circuit ? Give the working of a Full Wave Voltage Doubler.
4. Derive Diode equation for p-n junction. $2 \times 5 = 10$

SECTION—B

5. What are Photo conductive devices ? Explain any one of them.
6. What are the various configurations of a transistor ? Explain the Active, Cutoff and Saturation regions in the Output characteristic of a transistor in C.B. mode.